

## S.Y.B.Tech.(E & TC Engg.) (Sem-IV)

### End Semester Examination, July- 2023

Course Name :	Electronic Devices and Circuits-II	Course Code: ETC401
Day & Date :	<b>Tuesday, 4-Jul-2023</b>	Max Marks : 60 Marks
Time :	<b>10:00 am to 12:00 pm</b>	


- Instructions:**
- All questions are compulsory.
  - Figures to the right indicates full marks, Course Outcome (CO) & Bloom's Taxonomy Level (BL) (L1-Remembering, L2- Understanding, L3 – Applying, L4 – Analyzing, L5 – Evaluating, L6 - Creating)
  - Use of non-programmable calculator is allowed.
  - Assume suitable data if required. e) Standard Data sheet is allowed.

	Marks	B.L	CO
<b>Q.1 Attempt any two.</b>	<b>12</b>		
a) Compare all negative types of feedback for Amplifier Characteristics. (Draw table)		L1	1
b) For Current Series Feedback amplifier, $h_{fe}=50$ , $h_{ie}=1k\Omega$ , $R_L=1k\Omega$ , $R_e=100$ , $R=R_1 \parallel R_2=10K\Omega$ , Calculate feedback factor 'k' and $R_{if}$ .		L5	1
c) Design a two stage RC coupled amplifier to meet the following specifications. Load resistance- $2k\Omega$ , Source resistance- $600\Omega$ , Frequency range- $20Hz$ to $20KHz$ , Voltage gain per stage $>60$ , Supply voltage- $15V$ .		L4	2
<b>Q.2 Attempt any two.</b>	<b>12</b>		
a) Compare Class A, B, AB and C power amplifier.		L1	1
b) With waveform explain Cross-over distortion. How to avoid it.		L2	2
c) Design phase shift Oscillator for the following Specification: Peak to Peak Output amplitude = $5V$ , Frequency of Oscillation (f) = $10 KHz$ , Use $V_{cc} = 10V$ , $R_L=5K\Omega$ .		L5	3
<b>Q.3 Attempt any two.</b>	<b>12</b>		
a) Draw and explain with waveforms Monostable Multivibrator.		L2	2
b) Design an Astable multivibrator for frequency of $400Hz$ to give output voltage of $14 V$ . Use transistor BC 547 with: $P_D (MAX) = 500mW$ , $V_{CE} (sat) = 0.3V$ , $I_C (sat) = 5mA$ , $h_{fe} (Min) = 50$ .		L5	
c) Compare Astable, Monostable and Bistable Multivibrator.		L6	4
<b>Q.4 Attempt any two.</b>	<b>12</b>		
a) State the important features of IC78XX series.		L1	3
b) Draw & Explain the internal block diagram of IC79XX series voltage regulator.		L2	2
c) Draw & Explain the internal block diagram of IC78XX series voltage regulator.		L2	3

**Q.5 Attempt any two.**

**12**

- |  |           |          |
|--|-----------|----------|
| a) Draw the circuit diagram of two stages RC coupled amplifier and explain in brief.   | <b>L1</b> | <b>4</b> |
| b) An amplifier has mid frequency gain of 100 and a bandwidth of 200 KHz.<br>i) What will be the new bandwidth and gain if 5% feedback is introduced?<br>ii) What should be the amount of negative feedback if the bandwidth is to be restricted to 1 MHz? | <b>L6</b> | <b>3</b> |
| c) Derive the expression for efficiency of Class A transformer coupled power amplifier   | <b>L3</b> | <b>3</b> |
| d) Derive the equation for $A_{vf}$ with positive feedback and state Barkhausen's Criteria for Oscillator.   | <b>L1</b> | <b>2</b> |

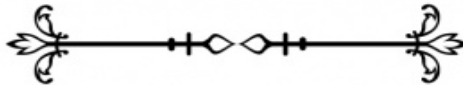

**S.Y.B.Tech.(E & TC Engg.) (Sem-IV)****End Semester Examination, July- 2023**

Course Name : Communication Engineering

Course Code: ETC402


Day & Date : **Thursday, 6-Jul-2023**

Max Marks : 60 Marks

Time : **10:00 am to 12:00 pm**

- Instructions:**
- All questions are compulsory
  - Figures to the right indicates full marks, Course Outcome (CO) & Bloom's Taxonomy Level (BL) (L1-Remembering, L2- Understanding, L3 – Applying, L4 – Analyzing, L5 – Evaluating, L6 - Creating)
  - Use of non-programmable calculator is allowed
  - Assume suitable data if required.

	Marks	B.L	CO
<b>Q.1 Attempt any two</b>	<b>12</b>		
a) Draw & explain basic block diagram of communication system.		<b>L1</b>	<b>1</b>
b) Draw & explain basic reactance modulator for the generation of FM.		<b>L2</b>	<b>1</b>
c) A 400W carrier is modulated to a depth of 75%. Calculate the total power in the modulated wave.		<b>L5</b>	<b>3</b>
<b>Q.2 Attempt any two</b>	<b>12</b>		
a) Explain different sources of noise.		<b>L1</b>	<b>4</b>
b) Draw & explain the block diagram of tuned radio frequency (TRF) receiver.		<b>L2</b>	<b>2</b>
c) If the resistor is operating at 27 <sup>0</sup> C and the bandwidth of interest is 2 MHz, then what is the maximum noise power output of a resistor?		<b>L5</b>	<b>3</b>
<b>Q.3 Attempt any two</b>	<b>12</b>		
a) Draw & explain ratio detector with its output equation.		<b>L4</b>	<b>2</b>
b) Draw & explain balanced slope detector with output waveform.		<b>L2</b>	<b>2</b>
c) Draw & explain amplitude limiting circuit with response characteristics.		<b>L2</b>	<b>1</b>
<b>Q.4 Attempt any two</b>	<b>12</b>		
a) Explain generation of PWM signal with neat circuit diagram and waveform.		<b>L2</b>	<b>2</b>
b) State and prove sampling theorem.		<b>L4</b>	<b>1</b>
c) Explain time division multiplexed PAM system.		<b>L2</b>	<b>2</b>
<b>Q.5 Attempt any two</b>	<b>12</b>		
a) Draw & explain suppression of carrier using balanced modulator.		<b>L2</b>	<b>2</b>
b) Differentiate between Narrowband FM & Wide Band FM		<b>L1</b>	<b>1</b>
c) Explain natural sampling along its waveform.		<b>L2</b>	<b>2</b>
d) Define following receiver parameters:		<b>L2</b>	<b>1</b>
a) Selectivity b) Sensitivity c) Fidelity			

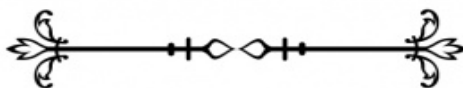

**S.Y.B.Tech.(E & TC Engg.) (Sem-II)****End Semester Examination, July- 2023**

Course Name : Linear Integrated Circuit

Course Code:ETC403

Day & Date : **Saturday, 8-Jul-2023**

Max Marks


60 Marks

Time : **10:00 am to 12:00 pm**

- Instructions:**
- All questions are compulsory
  - Figures to the right indicates full marks, Course Outcome (CO) & Bloom's Taxonomy Level (BL)
  - Use of non-programmable calculator is allowed
  - Assume suitable data if required.

		Marks	B.L.	CO
<b>Q.1</b>	<b>Attempt any two</b>	<b>12</b>		
a)	Determine $I_C$ , $V_{CE}$ , voltage Gain $A$ , i/p resistance $R_i$ & o/p resistance $R_o$ for DIBO differential amplifier if $R_C = 2.2K\Omega$ , $R_E = 4.7K\Omega$ , $V_{CC} = 10V$ , $V_{EE} = -10V$ , $\beta = 100$ & $V_{BE} = 0.7V$ .		<b>L5</b>	<b>1</b>
b)	Explain & analyze current mirror circuit.		<b>L4</b>	<b>2</b>
c)	Analyze DIBO configuration of differential amplifier (DC Analysis).		<b>L4</b>	<b>1</b>
<b>Q.2</b>	<b>Attempt any two</b>	<b>12</b>		
a)	Determine closed loop parameters $A_F$ , $R_{iF}$ , $R_{oF}$ , $F_F$ & $V_{OOT}$ for inverting amplifier if $R_1 = 470\Omega$ , $R_F = 4.7K\Omega$ , $R_i = 2M\Omega$ , $R_o = 75\Omega$ , $F_o = 5$ Hz, $A = 2 \times 10^5$ , $V_{CC} = 15V$ , $V_{EE} = -15V$ & $V_{sat} = \pm 13V$ .		<b>L5</b>	<b>2</b>
b)	Explain inverting summing amplifier as summer and averaging circuit for three input signals $V_a$ , $V_b$ and $V_c$ .		<b>L2</b>	<b>3</b>
c)	Explain V-to-I converter with grounded load and floating load.		<b>L2</b>	<b>2</b>
<b>Q.3</b>	<b>Attempt any two</b>	<b>12</b>		
a)	Design following oscillator circuits for oscillating frequency $f_o = 1KHz$ <ol style="list-style-type: none"> <li>RC phase shift oscillator with <math>C = 0.1\mu F</math></li> <li>Wein bridge oscillator with <math>C = 0.05\mu F</math></li> </ol>		<b>L1</b>	<b>4</b>
b)	Design 1 <sup>st</sup> order wide band pass filter with $f_L = 200Hz$ , $f_H = 1KHz$ & pass band gain of 4. Also determine Q factor. Select $C = 0.05\mu F$		<b>L3</b>	<b>4</b>
c)	Draw Logarithmic amplifier and show that output voltage is log function of input signal		<b>L2</b>	<b>4</b>

<b>Q.4</b>	<b>Attempt any two</b>	<b>12</b>		
a)	Draw and explain sample and hold circuit with waveform		<b>L5</b>	<b>5</b>
b)	With neat circuit diagram and waveform explain how square waveform is generated using op-amp.		<b>L5</b>	<b>5</b>
c)	Design square wave generator of frequency $f_0 = 1\text{KHz}$		<b>L5</b>	<b>5</b>
<b>Q.5</b>	<b>Attempt any two (Unit 1 to Unit 6)</b>	<b>12</b>		
a)	Derive the equation of differential gain of differential amplifier using op-amp		<b>L3</b>	<b>1</b>
b)	Draw instrumentation amplifier using transducer bridge and show that output voltage is directly proportional to the change in resistance of the transducer.		<b>L2</b>	<b>3</b>
c)	For all pass filter with $f=1\text{KHz}$ , $R=15.9\text{K}$ , $C=0.001\mu\text{F}$ , find phase angle.		<b>L4</b>	<b>2</b>

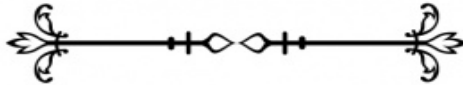

**S.Y.B.Tech.(All Branches) (Sem-II)**

**End Semester Examination, July-2023**

**Course Name :** (Control System Engineering)

**Course Code** ETC-404

**Day & Date :** Tuesday, 11-Jul-2023

**Max Marks** 60 Marks

**Time :** 10:00 am to 12:00 pm

- Instructions:**
- All questions are compulsory
  - Figures to the right indicates full marks, Course Outcome (CO) & Bloom's Taxonomy Level (BL)(L1-Remembering, L2- Understanding, L3 – Applying, L4 – Analyzing, L5 – Evaluating, L6 - Creating)
  - Use of non-programmable calculator is allowed
  - Assume suitable data if required.

	Marks	B.L	CO
<b>Q.1 Attempt any two</b>	<b>12</b>		
a) Explain mathematical modeling of rotational mechanical system.		L2	1
b) Define Time Response .Explain time response of 1 <sup>st</sup> order System for step input.		L2	2
c) Find overall transfer function C(S)/ R(S) of SFG.		L4	2
<b>Q.2 Attempt any two</b>	<b>12</b>		
a) Comment on system stability using routh's criterion. $S^5+2S^4+3S^3+6S^2+5S+3=0$ .		L4	3
b) Write Rules of Root Locus.		L2	3
c) Sketch polar plot of $G(S)=1/(s+4)(s+2)$			3
<b>Q.3 Attempt any two</b>	<b>12</b>		
a) Explain state ,state variable and state model.		L2	4
b) Explain frequency domain specifications.		L2	4
c) Plot bode plot of $G(s)=10/s(1+0.5s)(1+0.1s)$		L4	4
<b>Q.4 Attempt any two</b>	<b>12</b>		
a) Define Compensator and Explain Lead Compensator.		L2	4
b) Explain PLC with neat block diagram.		L2	4

c) Find error constants  $G(s)H(s)=s(s+4)/s(s^3+6s^2+8s)$ .


L4 3

**Q.5 Attempt any two**

12

a) Find  $C(S)/ R(S)$  using block diagram rules.

L2 1

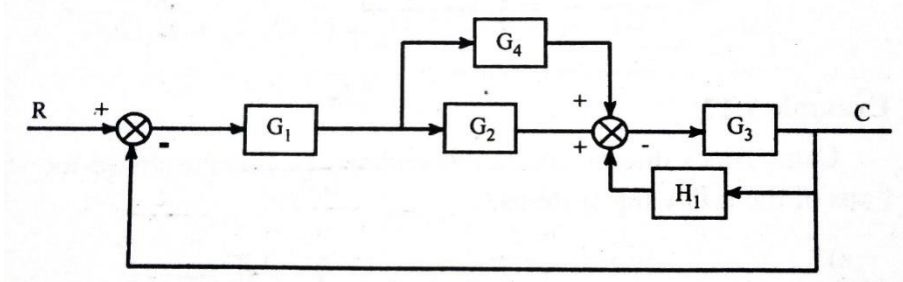

b) Explain Steady State Error and Error Constants.

L2 3


c) Comment on system stability using routh's criterion.

L4 3

$$s^6+2s^5+8s^4+15s^3+20s^2+16s+16=0$$

d) Explain PID Controller.

L2 4

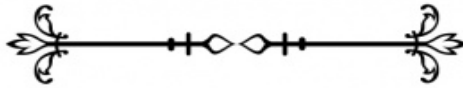


## S.Y.B.Tech.(E & TC Engg.) (Sem-IV)

### End Semester Examination, July- 2023

Course Name :	Data Structure & Algorithms	Course Code: ETC 405
Day & Date :	<b>Thursday, 13-Jul-2023</b>	Max Marks : 60 Marks
Time :	<b>10:00 am to 12:00 pm</b>	

- Instructions:**
- a) All questions are compulsory
  - b) Figures to the right indicates full marks, Course Outcome (CO) & Bloom's Taxonomy Level (BL)  
(L1-Remembering, L2- Understanding, L3 – Applying, L4 – Analyzing, L5 – Evaluating, L6 - Creating)
  - c) Use of non-programmable calculator is allowed
  - d) Assume suitable data if required.

	Marks	B.L	CO
<b>Q.1 Attempt any two</b>	<b>12</b>		
a) What is Data structure ?What are types of data structures ?		L1	3
b) What is record ? Explain record structure .		L2	1
c) Write an algorithm for traversing linear array.		L1	2
<b>Q.2 Attempt any two</b>	<b>12</b>		
a) What is linked list ?Differentiate array & linked list		L3	4
b) What is Stack ? What are different operations on stack ?		L2	1
c) Write an algorithm for Push & Pop operations		L1	3
<b>Q.3 Attempt any two</b>	<b>12</b>		
a) What is binary trees ? How to represent binary trees in memory ?		L6	3
b) What are different traversal methods used in Binary trees.		L4	2
c) Write an algorithm for traversing Linked list		L1	2
<b>Q.4 Attempt any two</b>	<b>12</b>		
a) What is graph ? What are different types of graphs ?		L2	2
b) Explain BFS traversing method for graph.		L5	3
c) What is linear searching ? What is complexity of Linear searching ?		L6	2
<b>Q.5 Attempt any two (Unit 1 to Unit 6)</b>	<b>12</b>		
a) What are different Data structure operations ?		L1	1
b) Explain sparse Matrices.		L2	2
c) What is recursion ? Write an algorithm for recursion		L4	2
d) Explain Header linked list		L6	4
		L1	3

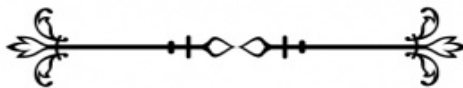




## T.Y.B.Tech.(All Branches) (Sem-II)

### End Semester Examination, July- 2023

Course Name :	Signal Processing	Course Code:ETC601	
Day & Date :	Monday, 3-Jul-2023	Max Marks	60 Marks
Time :	10:00 am to 12:00 pm		

- Instructions:**
- All questions are compulsory
  - Figures to the right indicates full marks, Course Outcome (CO) & Bloom's Taxonomy Level (BL)  
(L1-Remembering, L2- Understanding, L3 – Applying, L4 – Analyzing, L5 – Evaluating, L6 - Creating)
  - Use of non-programmable calculator is allowed
  - Assume suitable data if required.

	Marks	B.L	CO
<b>Q.1 Attempt any two</b>	<b>12</b>		
a) Explain properties of signals		L1	1
b) Explain Fourier Transform and its properties		L1	2
c) Explain stability of system and its impulse response		L1	1
<b>Q.2 Attempt any two</b>	<b>12</b>		
a) Draw signal flow graph for 8-Point Radix-2 DIF FFT		L3	2
b) Explain Frequency sampling method for FIR filter design.		L3	3
c) If $x(n)=\{1, 2, 1, 2\}$ find its DFT		L3	2
<b>Q.3 Attempt any two</b>	<b>12</b>		
a) Explain ROC and properties of ROC		L1	4
b) If $x(n)=\{1,2,3,4\}$ , find its ZT $X(z)$		L3	4
c) Explain ZT of Unit step and its ROC		L2	4
<b>Q.4 Attempt any two</b>	<b>12</b>		
a) Explain Direct Form-II realization of System		L1	5
b) Explain realization of typical second order System		L1	5
c) Explain Cascade Form realization of System		L1	5
<b>Q.5 Attempt any two (Unit 1 to Unit 6)</b>	<b>12</b>		
a) If $x(t)=e^{j(\pi/6)t}$ find whether it is periodic or not. If yes find its period.		L3	1
b) Explain Bilinear Transformation		L2	3
c) Explain DFT using Twiddle Factor		L1	2
d) Explain s-plan to z-plan mapping.			

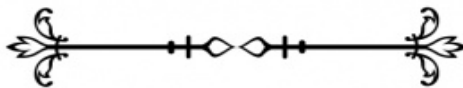


**T.Y.B.Tech.(E & TC Engg.) (Sem-VI)****End Semester Examination, July- 2023**Course Name : **Power Electronics**Course Code: **ETC602**Day & Date : **Wednesday, 5-Jul-2023**Max Marks : **60 Marks**Time : **2:00 pm to 4:00 pm**

- Instructions:**
- All questions are compulsory
  - Figures to the right indicates full marks, Course Outcome (CO) & Bloom's Taxonomy Level (BL) (L1-Remembering, L2- Understanding, L3 – Applying, L4 – Analyzing, L5 – Evaluating, L6 - Creating)
  - Use of non-programmable calculator is allowed
  - Assume suitable data if required.

		Marks	B.L	CO
<b>Q.1</b>	<b>Attempt any two</b>	<b>12</b>		
a)	Draw static characteristics of SCR. Define latching current, holding current, forward breakover voltage with reference to SCR	<b>6</b>	<b>L1</b>	<b>1</b>
b)	With the help of circuit diagram explain how dv/dt and di/dt protection is achieved in SCR.	<b>6</b>	<b>L1,L2</b>	<b>1</b>
c)	With the help of block diagram and waveform explain cosine based firing circuit.	<b>6</b>	<b>L1</b>	<b>1</b>
<b>Q.2</b>	<b>Attempt any two</b>	<b>12</b>		
a)	Explain with necessary waveforms single phase bridge converter with R load. Derive the equation of average output voltage.	<b>6</b>	<b>L1</b>	<b>2</b>
b)	For 230V,1 phase semiconverter with RL load, load current is continuous and ripple free. It is observed that average output voltage is 50% that of maximum possible average output voltage. Calculate: i) firing angle ii) Average output vol. iii) RMS output vol. iv) Rectification efficiency.	<b>6</b>	<b>L5</b>	<b>2</b>
c)	Explain in detail operation of single-phase full bridge inverter with R load. Also derive the equation of rms output voltage.	<b>6</b>	<b>L1</b>	<b>2</b>
<b>Q.3</b>	<b>Attempt any two</b>	<b>12</b>		
a)	Explain the operation of step down chopper with R load. Derive the equation of output voltage.	<b>6</b>	<b>L1</b>	<b>3</b>
b)	Explain the control techniques of chopper.	<b>6</b>	<b>L1</b>	<b>3</b>
c)	Explain the operation of step up chopper and derive the equation of output voltage.	<b>6</b>	<b>L1</b>	<b>3</b>
<b>Q.4</b>	<b>Attempt any two</b>	<b>12</b>		
a)	Draw and explain characteristics of DC motor.	<b>6</b>	<b>L1,L2</b>	<b>4</b>
b)	Explain single phase full converter drives.	<b>6</b>	<b>L1</b>	<b>4</b>
c)	Explain speed torque characteristics of induction motor.	<b>6</b>	<b>L1</b>	<b>4</b>
<b>Q.5</b>	<b>Attempt any two (Unit 1 to Unit 6)</b>	<b>12</b>		

- |   |          |           |          |
|---|----------|-----------|----------|
| a) Explain different voltage control technique of inverter.     | <b>6</b> | <b>L1</b> | <b>3</b> |
| b) Explain construction detail & VI characteristic of TRIAC.    | <b>6</b> | <b>L1</b> | <b>1</b> |
| c) Differentiate forced and natural commutation methods of SCR. | <b>6</b> | <b>L1</b> | <b>2</b> |

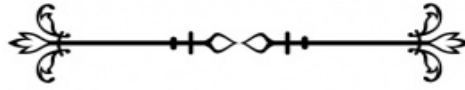


**T.Y.B.Tech.(E & TC Engg.) (Sem-II)****End Semester Examination, July- 2023**

Course Name : ANTENNA AND WAVE PROPAGATION Course Code: ETC603  
 Day & Date : **Friday, 7-Jul-2023** Max Marks : 60 Marks  
 Time : **2:00 pm to 4:00 pm**

- Instructions:**
- All questions are compulsory
  - Figures to the right indicates full marks, Course Outcome (CO) & Bloom's Taxonomy Level (BL) (L1-Remembering, L2- Understanding, L3 – Applying, L4 – Analyzing, L5 – Evaluating, L6 - Creating)
  - Use of non-programmable calculator is allowed
  - Assume suitable data if required.

	<b>Marks</b>	<b>B.L</b>	<b>CO</b>
<b>Q.1 Attempt any two</b>	<b>12</b>		
a) Derive Friss formula of radio communication link		<b>L5</b>	<b>CO1</b>
b) Calculate maximum effective aperture of antenna which is operating at wavelength of 2 m and directivity 100		<b>L5</b>	<b>CO2</b>
c) Derive the expression to calculate the field at far point due to array of two point sources with equal amplitude and opposite phase		<b>L4</b>	<b>CO3</b>
<b>Q.2 Attempt any two</b>	<b>12</b>		
a) With diagram explain Log periodic antenna.		<b>L2</b>	<b>CO1</b>
b) Explain how the reflection of EM waves varies with roughness of earth		<b>L1</b>	<b>CO2</b>
c) Write note on Radio horizon of antenna and derive the expression for radio horizon distance		<b>L1</b>	<b>CO3</b>
<b>Q.3 Attempt any two</b>	<b>12</b>		
a) Explain the ionosphere structure		<b>L1</b>	<b>CO1</b>
b) Explain virtual height concept		<b>L5</b>	<b>CO2</b>
c) Define (i) Critical frequency (ii) Maximum Usable Frequency		<b>L4</b>	<b>CO3</b>
<b>Q.4 Attempt any two</b>	<b>12</b>		
a) Explain basic principle of RADAR		<b>L2</b>	<b>CO1</b>
b) Derive RADAR range equation		<b>L5</b>	<b>CO3</b>
c) Describe the applications of RADAR.		<b>L1</b>	<b>CO2</b>
<b>Q.5 Attempt any two</b>	<b>12</b>		
a) Explain ionosphere and its irregular variations		<b>L1</b>	<b>CO1</b>
b) Briefly explain parameters which affect the field strength in space wave propagation		<b>L4</b>	<b>CO3</b>
c) Write note on polarization of antenna.		<b>L1</b>	<b>CO2</b>
d) What are the factors which affects ionosphere propagation		<b>L4</b>	<b>CO2</b>

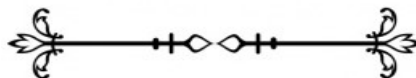

Seat No.	
----------	--

**Tatyasaheb Kore Institute of Engineering and Technology, Warananagar**  
(An Autonomous Institute, Affiliated to Shivaji University, Kolhapur)

**T.Y.B.Tech.(E & TC Engg.) (Sem-VI)**  
**End Semester Examination, July- 2023**

Course Name : Embedded Systems  
Day & Date : **Monday, 10-Jul-2023**  
Time : **2:00 pm to 4:00 pm**

Course Code: ETC-604  
Max Marks : 60 Marks

- Instructions:**
- a) All questions are compulsory
  - b) Figures to the right indicates full marks, Course Outcome (CO) & Bloom's Taxonomy Level (BL)  
(L1-Remembering, L2- Understanding, L3 – Applying, L4 – Analyzing, L5 – Evaluating, L6 - Creating)
  - c) Use of non-programmable calculator is allowed
  - d) Assume suitable data if required.

		Marks	B.L	CO
<b>Q.1</b>	<b>Attempt any two</b>	<b>12</b>		
a)	Differentiate RISC & CISC architecture..		<b>L1</b>	<b>3</b>
b)	Draw & explain ARM core data flow model.		<b>L2</b>	<b>1</b>
c)	Draw & explain CPSR register		<b>L1</b>	<b>2</b>
<b>Q.2</b>	<b>Attempt any two</b>	<b>12</b>		
a)	Draw & explain RS-232.		<b>L3</b>	<b>4</b>
b)	Draw & explain memory organization of LPC 2148		<b>L2</b>	<b>1</b>
c)	Write Arithmetic & logical instruction set of ARM.		<b>L1</b>	<b>3</b>
<b>Q.3</b>	<b>Attempt any two</b>	<b>12</b>		
a)	What are features of LPC 2148 ?		<b>L6</b>	<b>3</b>
b)	What are features of ADC used in LPC 2148		<b>L4</b>	<b>2</b>
c)	What are Features of GPIO used in LPC 2148		<b>L1</b>	<b>2</b>
<b>Q.4</b>	<b>Attempt any two</b>	<b>12</b>		
a)	Write a program for Stepper motor interfacing .		<b>L2</b>	<b>2</b>
b)	Draw & explain CAN bus		<b>L5</b>	<b>3</b>
c)	Draw & explain IIC bus.		<b>L6</b>	<b>2</b>
<b>Q.5</b>	<b>Attempt any two</b>	<b>12</b>		
a)	Differentiate Von Neuman & Harward architecture .		<b>L1</b>	<b>1</b>
b)	What is Embedded system ? What are types of Embedded systems ?		<b>L2</b>	<b>2</b>
c)	What is barallel shifter ?Write barallel shifter instructions		<b>L4</b>	<b>2</b>
d)	What are different ARM operating modes ?		<b>L6</b>	<b>4</b>



**T.Y.B.Tech.(E & TC Engg.) (Sem-VI)****End Semester Examination, July- 2023**

Course Name :	MOBILE TECHNOLOGY (OE-II)	Course Code:	ETC605
Day & Date :	<b>Wednesday, 12-Jul-2023</b>	Max Marks :	60 Marks
Time :	<b>2:00 pm to 4:00 pm</b>		

- Instructions:**
- All questions are compulsory
  - Figures to the right indicates full marks, Course Outcome (CO) & Bloom's Taxonomy Level (BL)  
(L1-Remembering, L2- Understanding, L3 – Applying, L4 – Analyzing, L5 – Evaluating, L6 - Creating)
  - Use of non-programmable calculator is allowed
  - Assume suitable data if required.

		Marks	B.L	CO
<b>Q.1</b>	<b>Attempt any two</b>	<b>12</b>		
	a) Compare the different mobile generations.	<b>6</b>	<b>L4</b>	<b>CO2</b>
	b) Explain the frequency reuse concept in detail.	<b>6</b>	<b>L2</b>	<b>CO1</b>
	c) Differentiate between cellular network and adhoc network.	<b>6</b>	<b>L1</b>	<b>CO1</b>
<b>Q.2</b>	<b>Attempt any two</b>	<b>12</b>		
	a) Draw the diagram and explain architecture of GSM.	<b>6</b>	<b>L1</b>	<b>CO1</b>
	b) What is need for agent discovery & what is agent solicitation?	<b>6</b>	<b>L1</b>	<b>CO3</b>
	c) What is MSISDN, IMSI, TMSI, MSRN.	<b>6</b>	<b>L1</b>	<b>CO1</b>
<b>Q.3</b>	<b>Attempt any two</b>	<b>12</b>		
	a) Explain the slow start mechanism in detail.	<b>6</b>	<b>L1</b>	<b>CO3</b>
	b) Briefly discuss the M-TCP approach in mobile wireless network.	<b>6</b>	<b>L2</b>	<b>CO3</b>
	c) How does I-TCP isolate problem on the wireless link.	<b>6</b>	<b>L2</b>	<b>CO3</b>
<b>Q.4</b>	<b>Attempt any two</b>	<b>12</b>		
	a) Draw the diagram and explain the architecture of WAP (Wireless Application Protocol).	<b>6</b>	<b>L1</b>	<b>CO4</b>
	b) State the advantages and limitations of WAP.	<b>6</b>	<b>L4</b>	<b>CO4</b>
	c) What are the various protocols in a WAP protocol suite	<b>6</b>	<b>L1</b>	<b>CO4</b>
<b>Q.5</b>	<b>Attempt any two</b>	<b>12</b>		
	a) Explain the following entities associated with mobile IP.	<b>6</b>	<b>L1</b>	<b>CO3</b>
	a) Mobile Node                      b) Correspondent Node                      c) Home Network			
	d) Foreign Network                      e) Home Agent                      f) Foreign Agent			
	b) Explain the different signal propagation effects	<b>6</b>	<b>L2</b>	<b>CO1</b>
	c) Explain adjacent channel interference and co-channel interference.		<b>L2</b>	<b>CO1</b>
	d) Write short note on security in GSM.	<b>6</b>	<b>L1</b>	<b>CO1</b>



**T.Y.B.Tech.(E & TC Engg.) (Sem-VI)****End Semester Examination, July- 2023**

Course Name : Cyber Security and Law

Course Code: ETC-H-601

Day & Date : **Friday, 14-Jul-2023**

Max Marks : 60 Marks

Time : **2:00 pm to 4:00 pm**

- Instructions:**
- All questions are compulsory
  - Figures to the right indicates full marks, Course Outcome (CO) & Bloom's Taxonomy Level (BL) (L1-Remembering, L2- Understanding, L3 – Applying, L4 – Analyzing, L5 – Evaluating, L6 - Creating)
  - Use of non-programmable calculator is allowed
  - Assume suitable data if required.

	Marks	B.L	CO
<b>Q.1 Attempt any two</b>	<b>12</b>		
a) How to evaluate cyber stalking?		<b>L4</b>	<b>1</b>
b) Explain port scanning active scanning techniques		<b>L3</b>	<b>2</b>
c) Explain spyware & legal uses of spyware.		<b>L2</b>	<b>2</b>
<b>Q.2 Attempt any two</b>	<b>12</b>		
a) Define Cyber Physical System. Explain general workflow of cyber physical system.		<b>L2</b>	<b>2</b>
b) Explain general guidelines to follow in any forensic examination.		<b>L1</b>	<b>2</b>
c) Explain countermeasures in CPS.		<b>L2</b>	<b>2</b>
<b>Q.3 Attempt any two</b>	<b>12</b>		
a) Explain positive aspects of the ITA 2000.		<b>L1</b>	<b>3</b>
b) Explain challenges to Indian Law and cybercrime scenario in India.		<b>L2</b>	<b>3</b>
c) Explain sections 67, 71 of the Indian ITA 2000.		<b>L1</b>	<b>3</b>
<b>Q.4 Attempt any two</b>	<b>12</b>		
a) Explain in brief about cyber crime or offence. Give the name of different Act associated with cyber crime.		<b>L2</b>	<b>4</b>
b) Explain about different cyber security awareness tips.		<b>L2</b>	<b>4</b>
c) Explain classification of Intellectual Property.		<b>L1</b>	<b>4</b>
<b>Q.5 Attempt any two</b>	<b>12</b>		
a) Explain about how to detect & eliminate spyware & viruses.		<b>L4</b>	<b>1</b>
b) Explain Cross-Site Scripting attack.		<b>L2</b>	<b>2</b>
c) Draw technical architecture of Blockchain & explain its Core Components.		<b>L2</b>	<b>2</b>
d) Explain different operating system utilities that can be useful in gathering forensic data.		<b>L3</b>	<b>2</b>

