

Roll No	
----------------	--

**Tatyasaheb Kore Institute of Engineering & Technology, Warananagar
(An Autonomous Institute)**

F.Y. B. Tech (Sem-I), In Semester Examination –I, September 2023

BASIC ELECTRICAL & ELECTRONICS ENGINEERING

Day and Date: Wednesday, 27 September 2023

Marks: 30

Time : 9:15 am to 10:15 am

**Instructions: i) Use of non programmable calculator is allowed.
ii) Figures to the right indicate full marks.**

Q.1 Attempt any Three from the following questions.	Unit No	CO	
a) Define the following terms & write its unit i) EMF ii) Current iii) Potential difference	1	1	5
b) State & explain Kirchoff's Current & Voltage laws	1	1	5
c) Two batteries A & B are connected in parallel across a load resistance of 8Ω . The emf & internal resistance of battery A & B are 40V, 4Ω and 50V, 4Ω respectively, by using Node analysis method, Find. i) Current in battery A, ii) Current in battery B iii) Current in load resistance	1	1	5
d) Two batteries A & B are connected in parallel across a load resistance of 6Ω . The emf & internal resistance of battery A & B are 18V, 2Ω and 24V, 4Ω respectively, by using Mesh analysis method, Find. i) Current in battery A, ii) Current in battery B iii) Current in load resistance	1	1	5
 Q.2 Attempt any Three from the following questions.			
a) Define the following terms & write its unit i) MMF ii) Reluctance iii) Magnetic flux density	2	2	5
b) Obtain the mathematical expression for series magnetic circuit, prove that Total MMF = $H_i l_i + H_g l_g$	2	2	5
c) Two batteries A & B are connected in parallel across a load resistance of 10Ω . The emf & internal resistance of battery A & B are 34V, 6Ω and 46V, 6Ω respectively, by using Node/Mesh analysis method, Find. i) Current in battery A, ii) Current in battery B iii) Current in load resistance	2	2	5
d) Two batteries A & B are connected in parallel across a load resistance of 12Ω . The emf & internal resistance of battery A & B are 16V, 2Ω and 26V, 2Ω respectively, by using Node/Mesh analysis method, Find. i) Current in battery A, ii) Current in battery B iii) Current in load resistance	2	2	5