

Roll No	
---------	--

**TatyasahebKore Institute of Engineering & Technology, Warananagar
(An Autonomous Institute)**

F.Y.B.Tech(Sem-I), In Semester Examination –II, October 2023

BASIC ELECTRICAL & ELECTRONICS ENGINEERING

Day and Date: Saturday, 28 October 2023

Marks: 30

Time :9:15 am to 10:15 am

Instructions: i) Use of non programmable calculator is allowed.

ii) Figures to the right indicate full marks.

Q.1	Attempt any 3 from the following questions.	Unit No	CO	
a)	Explain operating principle of PN junction diode with neat symbol & V-I characteristics	3	3	5
b)	Explain operating principle of Full wave rectifier with neat circuit diagram & waveform	3	3	5
c)	What is transistor? Explain operation of PNP transistor with neat sketch	3	3	5
d)	A resistance of 22Ω is connected in series with inductance of 43.2mH across 220V , 50Hz supply. Find i) Inductive reactance ii) Impedance iii) Power consumed	3	3	5
Q.2	Attempt any 3 from the following questions.			
a)	Determine phase angle relationship between alternating voltage & current in a purely Resistive circuit & also prove that average power consumed in a circuit is $P=E*I$ Watt	4	4	5
b)	Derive an expression for R-L series circuit & draw phasor diagram	4	4	5
c)	A resistance of 15Ω is connected in series with capacitance of $520\mu\text{f}$, across 230V , 50Hz single phase AC supply. Find i) Impedance ii) Power factor iii) Power dissipation	4	4	5
d)	A resistance of 12Ω , inductance of 0.14H and capacitance of $150\mu\text{f}$ are connected in series across 200V , 50Hz supply then Find i) Impedance ii) current iii) Power consumed	4	4	5